

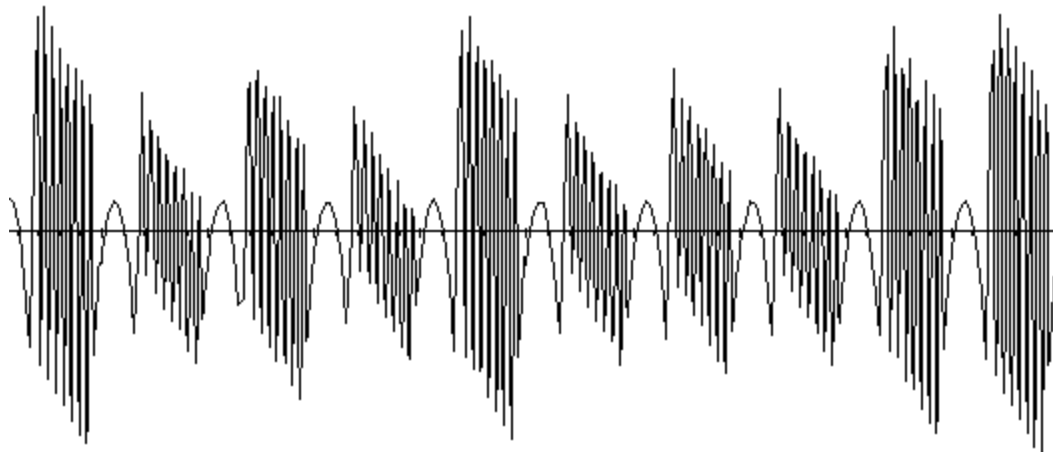
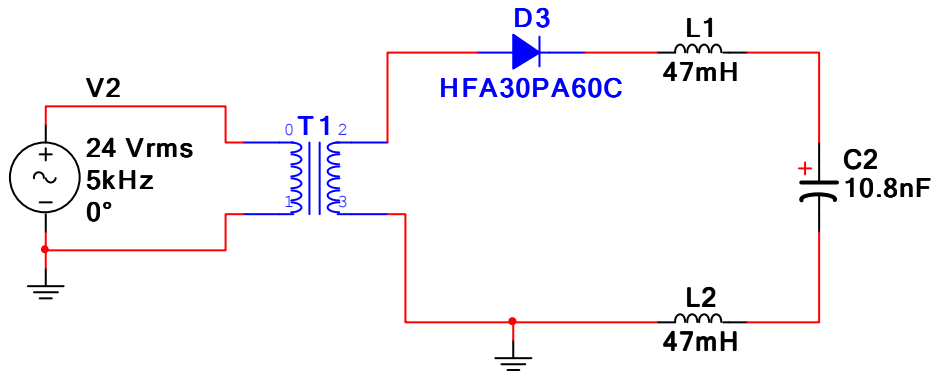
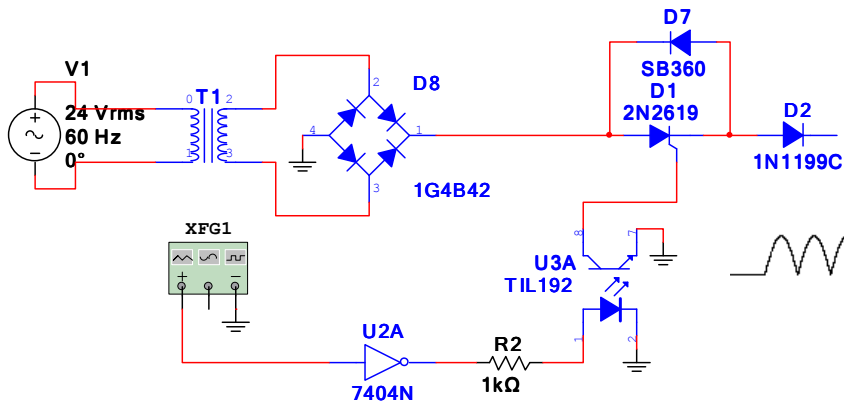




These are all the circuits that I've come up with to replicate the following waveforms:
Xogen, Stanley Meyer, & Henry Puharich.


Xogen Waveform

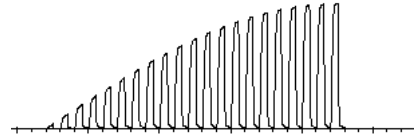

Stan Meyer Circuit

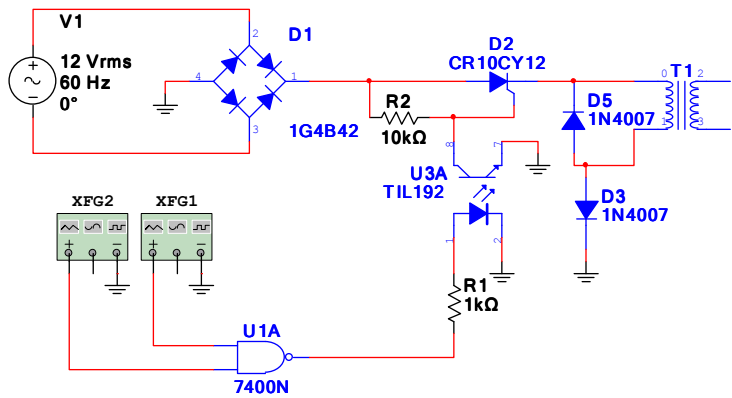

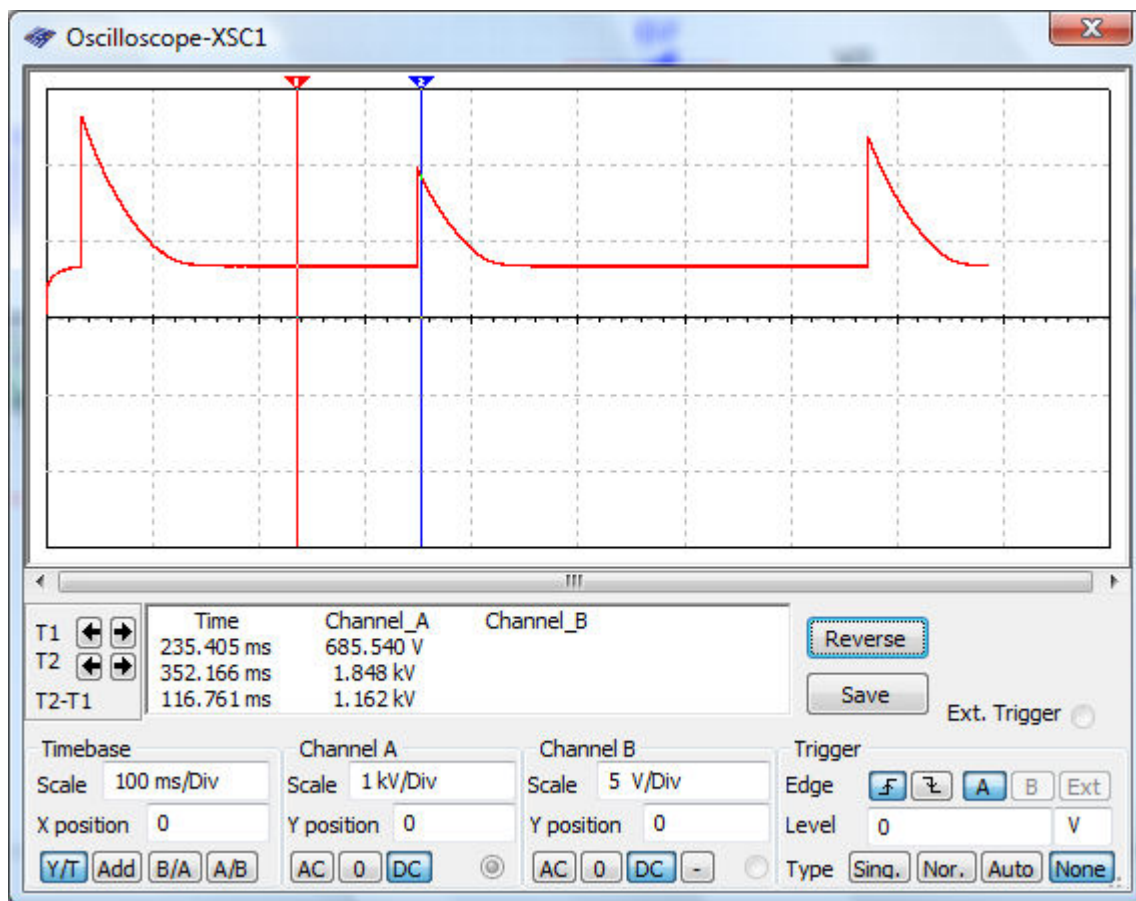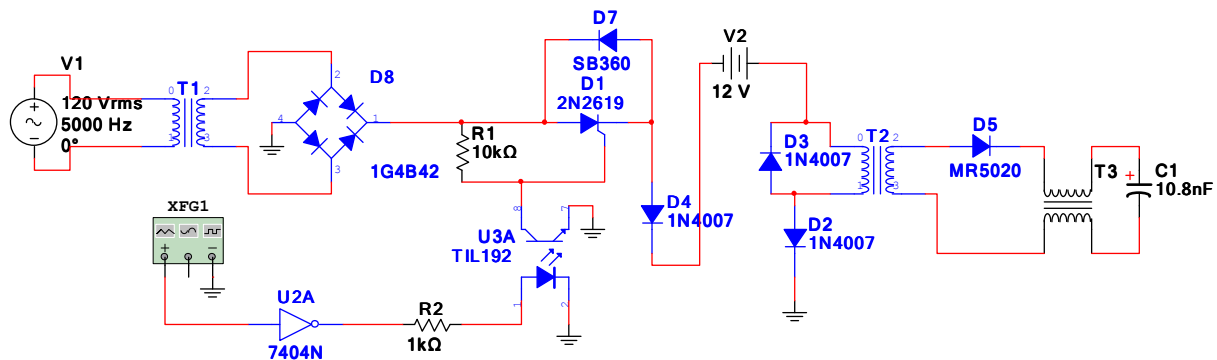

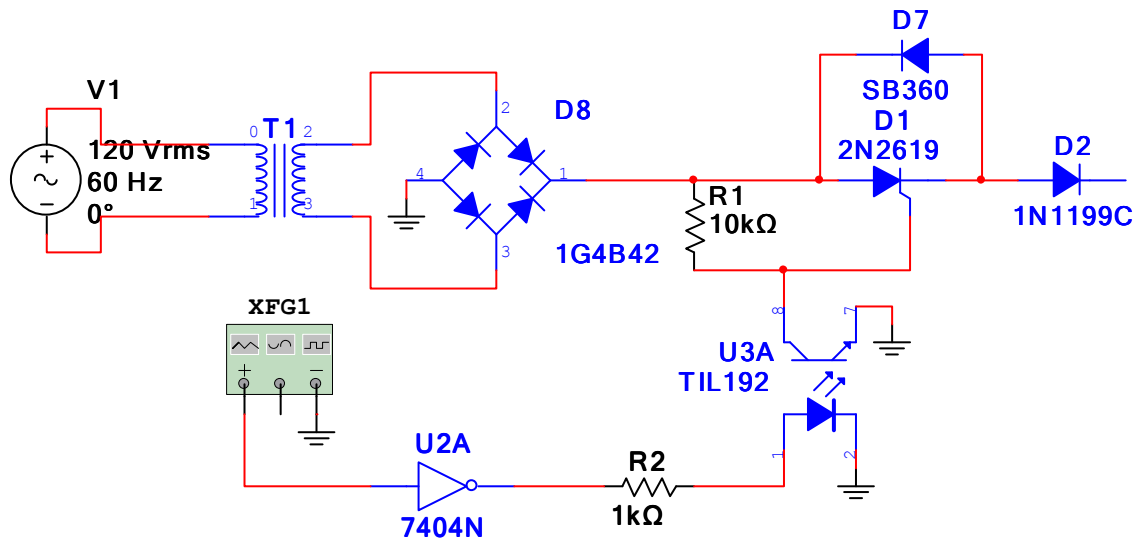

Henry Puharich Waveform

